Table of contents

- Table of contents
- Problem statement
- Analogues
- User guide
- Documentation
- Special terms
- Assembler
 - Short description
 - RAM distribution
 - Cells referring to I/O regs.
 - Code description
 - Simulation start
 - Main cycle
 - Subroutines
 - spreadByte
 - processBit
- Logisim
 - Main concept
 - Engine circuit
 - Coordinates bus
 - Controls
 - Main signals
 - Keyboard
 - Keyboard layouts
 - I/O registers
 - I/O registers' types
 - PSEUDO WRITE
 - Short description table
 - List with descriptions
 - Simulation rules
 - Processed cell
 - I/O "registers" with environment data
 - I/O "registers" for changing field
 - Elements description
 - Keyboard controller
 - Random write buffer
 - Stable generation's buffer
 - Row environment mask
 - Environment data constructor
 - Row's bit invertor
 - Binary selector
 - Blinker

Problem statement

Realization of "Conway game of life" using Logisim and Cdm-8.

"Conway Game of life" is a cellural automaton. This is a zero player game, player set an initial condition and then only can observe the development.

Rules:

- 1. The field of "Game of life" is a grid of square cells. Each cell has two conditions it can be live or dead.
- 2. Every cell has 8 neighbours, which are the cells that are horizontally, vertically, or diagonally adjacent.
- 3. Any live cell with less than two neighbours dies because of underpopulation.
- 4. Any dead cell with three neighbours becomes a live.
- 5. Any live cell with two or three neighbours continues to live.
- 6. Any live cell with more than three neighbours dies because of overpopulation.

We have made 2 powerful improvements and 2 concept changes from the basic technical task.

Improvements:

- 1. We have composed a toroidal cycled field with size 32*32
- 2. We have extended simulation rules choice using 2 8-bit inputs as bit-arrays. Now you can set birth or surviving for any combination of neighbors count from 1 to 8.

Concept changes:

- 1. We have decided to use Logisim keyboard handling circuit for cursor moving and cell changing instead of a joystick.
- 2. Video buffer (named random write buffer) has been made asynchronous. Besides, we have add clear input to it.

Other components wasn't mentioned in basic technical project. Here you can see our addition for the technical project.

Analogues

We have found 3 interesting versions of "Conway game of life" in the Internet

- 1. Version is full madden in Logisim with toroidal field 16*16. Works fast but small field doesn't allow construct a lot of setups. For example "Pulsar" or "Copperhead":
- 2. Web version fast and convenient. Has endless field. Alas, we do not have similar capacities
- 3. In this video you can see Turing machine, 1D and 3D version, CPU-like version and so on.

User guide


Our version of "Conway game of life" works with universal sets of conditions for birth and survival.

- 1. To set conditions switch bits in birth/survival 8-bit inputs where value 1 on position N means that birth/survival will be fulfilled when cell has N neighbors.
- 2. After this click on keyboard element and use one of two keyboard layouts to move blinking cursor and change cells' states.

DIRECTION	KEY	
bottom-left	NUM 1/Z	
bottom	NUM 2/S	
bottom-right	NUM 3/C	
left	NUM 4/A	
right	NUM 6/D	
top-left	NUM 7/Q	
top	NUM 8/W	
top-right	NUM 9/E	

NUM 5 / Space - change state of selected cell

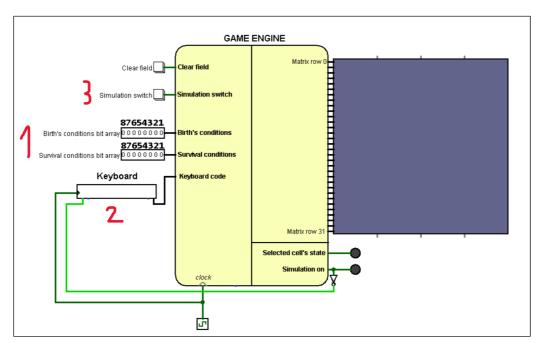3. When you have set initial field state press button "Simulation switch" and observe evolution! You can stop simulation and edit field at any time. But if CPU cursor has processed some cells you would get half-counted generation



Documentation

Special terms

There are some special terms that are used in different places below:

- 1. Environment is cell or cells' set with a border one cell wide on all sides. E.g.:
 - for cell (Y, X) environment will be [(Y-1, X-1), (Y-1, X), (Y-1, X+1), (Y, X-1), (Y, X), (Y, X+1), (Y+1, X-1), (Y+1, X), (Y+1, X+1)] with centre bit bit (Y, X) (term centre bit is meaningful only for one cell's environment)
 - environment for full row (all X in range [0, 31]) Y will be full rows Y-1, Y and Y+1
- 2. Environment sum is a sum of cells' values from environment border
- 3. **Significant environment** is an environment which has at least one cell with value 1 (including border cells)

Assembler

Short description

Due to optimization reasons CdM-8 has only one main task - iteration by Y,X positions and determination whether cell should be changed. After the all cells' processing CdM-8 send signal to [update generation]

In ASM code we use asect constants like this:

```
asect 8
constSample:
# ...

ldi r0, constSample # r0 sets to 8
```

Often we save address value to its address:

```
ldi r0, IOAddr
st r0, r0
```

The reason for this action is PSEUDO WRITE mode for some I/O registers

RAM distribution

- 0xe0 birth's conditions first byte
- 0xe8 death's conditions first byte

Stack initial position - 0xe0

▼ Constants for this cells

```
# Internal data addresses
asect 0xe0
birthConditionsRowStart:

asect 0xe8
deathConditionsRowStart:
```

Cells referring to I/O regs.

Cells from 0xf0 to 0xff are allocated for I/O registers.

See detailed description in Logisim topic

► Constants for I/O cells

```
# Asects for I/O registers
asect 0xf0
IOGameMode:
asect 0xf1
IOBirthConditions:
asect 0xf2
IODeathConditions:
asect 0xf3
IOY:
asect 0xf4
IOX:
asect 0xf5
IOBit:
asect 0xf6
IOEnvSum:
asect 0xf7
IONullRowsEnv:
asect 0xf8
IONextSignificantX:
asect 0xf9
IOInvertBitSignal:
asect 0xfa
IOUpdateGeneration:
```

Code description

Simulation start

This part just waits whilst user presses start button and after it loads game conditions to RAM using spreadByte subroutine

For optimized conditions checking survival conditions inverts to death's conditions. See how it works here

▶ Code

```
asect 0
br start
#=======#
    Place for subroutines
#=======#
start:
      # Move SP before I/O and field addresses
       setsp 0xd0
       # Waiting for IOGameMode I/O reg. != 0
      ldi r1, IOGameMode
       do
             ld r1, r0
             tst r0
       until nz
      ldi r1, gameMode
       st r1, r0
      # Read birth and death conditions from I/O regs.
      ldi r1, IOBirthConditions
      ld r1, r0
      ldi r1, birthConditionsRowStart
       jsr spreadByte
      ldi r1, IODeathConditions
      ld r1, r0
      ldi r1, deathConditionsRowStart
       jsr spreadByte
```

Main cycle

This part will repeats while simulations stays on.

Before cycle we update stable generation's buffer using save signal to IOUpdateGeneration referred to Logisim. As a result, we can get correct data for processing cells.

Main cycle iterates by Y (row index) in decreasing order [31, 0].

We use two optimizations for skipping meaningless iterations:

- 1. If rows Y-1, Y and Y+1 (rows environment) are null (flag from IONullRowsEnv referred to I/O register will be 1) \$\rArr\$ we decrement Y.
- 2. If rows environment isn't null we iterates by X with significant environment (surrounding sum > 0 or centre bit = 1) which are received from IONextSignificantX I/O register. When new received X >= current X we end cycle for this row

For every significant (Y, X) combination we get state of selected cell and its environment's sum using IOBit and IOEnvSum addresses which are referred to I/O registers

For zero sum:

- Alive cell is killed immediately using save signal IOInvertBitSignal referred to Logisim
- Empty cell is skipped

For non-zero sum we call subroutine processBit

► Code

```
main:
        # Update stable generation's buffer to get new data from env. data
        ldi r0, IOUpdateGeneration
        st r0, r0
        # Count new cells' states
        ldi r3, 31 # row iterator
                # If game mode = 0 we interrupt cycle and go to start code part
                # NEW GENERATION CAN BE COUNTED PARTITIONALLY
                ldi r0, IOGameMode
                ld r0, r0
                tst r0
                bz start
                push r3 # Save row iterator
                # Send Y to logisim
                ldi r0, IOY
                st r0, r3
```

```
# If all rows in env. are null => skip this row
                ldi r3, IONullRowsEnv
                ld r3, r3
                tst r3
                bnz rowProcessed
                ldi r1, 0 # Value for searching first significant X
                # Send X to Logisim
                ldi r0, IOX
                st r0, r1
                # Get the first X with significant env.
                ldi r3, IONextSignificantX
                ld r3, r2
                do
                        # Save currnt X
                        move r2, r1
                        push r1
                        # Send X to Logisim
                        ldi r0, IOX
                        st r0, r1
                        # Read data for this cell
                        ldi r0, IOEnvSum
                        ld r0, r0
                        ldi r1, IOBit
                        ld r1, r1
                        # Check birth or death conditions and save bit depends on
conditions
                        if
                                tst r0
                        is nz
                                jsr processBit
                        else
                                # If sum = 0 alive cell must die
                                        tst r1
                                is nz
                                        ldi r0, IOInvertBitSignal
                                        st r0, r0
                                fi
                        fi
                        # Get the next X with significant env. lower than current
                        pop r1
                        ld r3, r2
                        # If new X greater of equal => cycle ends
                        cmp r2, r1
                until ge
```

```
rowProcessed:

# Get and decrement row iterator

pop r3

dec r3

until mi

# Infinite simulation cycle
br main
```

Subroutines

spreadByte

- This subroutine spread byte from r0 into cells from r1 to r1 + 7. In other words spreadByte writes every bit of byte from r0 to cells from r1 to r1 + 7, writing the low order bit into r1 and the high oreder bit into r1 + 7.
- spreadByte is used to write game settings to the memory.
- Thanks to spreadByte we can easily decide what we should do with current cell without using loops.

▶ Code

```
spreadByte:
        # Iterator
        ldi r3, 0b00001000 # 8
        while
                tst r3
        is nz
                # The process of spreading byte
                # Get lower bit and save to current cell
                ldi r2, 0b00000001
                and r0, r2
                st r1, r2
                # Increment cell address, shift data byte and decrement iterator
                shra r0
                dec r3
        wend
rts
```

processBit

- This subroutine gets neighbors' sum in ro and centre bit value in r1.
- Depending on bit value it chooses birth or death conditions
- Thanks to spreaded conditions we can simply add to conditions' begin address value r0 1 and check data by new address
- If there is 1 we should change value in selected cell so we send this signal to Logisim

► Code

```
processBit:
    # r0 - sum
    # r1 - bit
    # Send save signal to PSEUDO reg. IOInvertBitSignal if bit should be
inverted (we count that IOX and IOY regs. contain correct coords.)
```

```
if
                tst r1
        is z
                ldi r2, birthConditionsRowStart
        else
                ldi r2, deathConditionsRowStart
        fi
        # Check bit in spreaded space
        dec r0
        add r0, r2
        ld r2, r2
        # If there is 1 than we switch bit
        if
                tst r2
        is nz
                ldi r0, IOInvertBitSignal
                st r0, r0
        fi
rts
```

What to do if there is no neighbors?

We decided that alive cell should die and death cell cannot birth. Due to specific work with sum = 0 this case for bit = 1 is processed in main part:

Back to table of contents


Logisim

Main concept


Here you can see main jobs for Logisim part and logical ordered references for all of them:

- 1. Communication with user
 - 1. Controls
 - 2. Game screen
 - 3. Blinker for pretty cursor visualization
- 2. Storing game's data
 - 1. Random write buffer
 - 2. Stable generation's buffer
- 3. Constructing data for CPU
 - 1. Used I/O registers: cell and environment data
 - 2. Environment data constructor
- 4. Creating new generation by CPU signals
 - 1. Used I/O registers: cell and signals
 - 2. Row's bit invertor
 - 3. Random write buffer
 - 4. Stable generation's buffer

Engine circuit

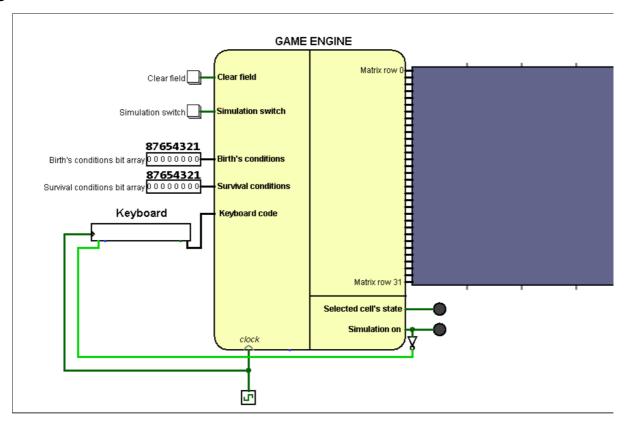


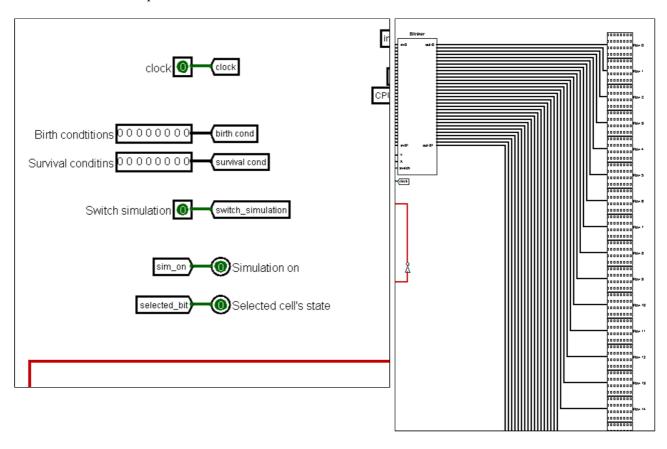This circuit is main one element of game. It handles all inputs from user and gives finally 32 32-bit rows to matrix and outputs simulation on and selected cell's state.




This circuit contains:

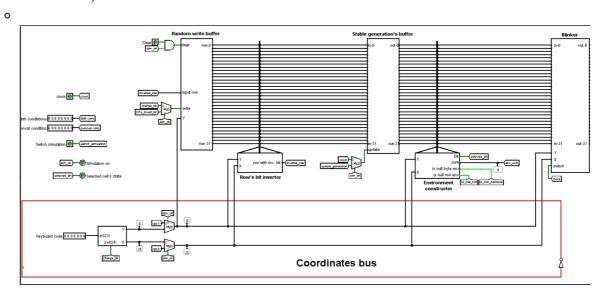
1. Most of all circuits below with connected to them coordinates bus (excepting binary selector and row environment mask):



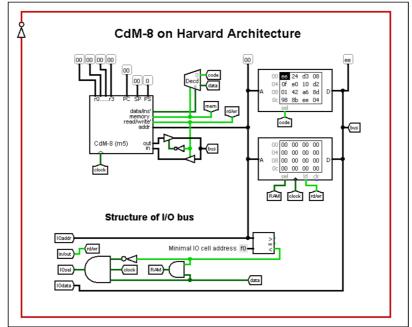2. CdM-8 integration scheme with Harvard architecture:



3. All I/O registers:

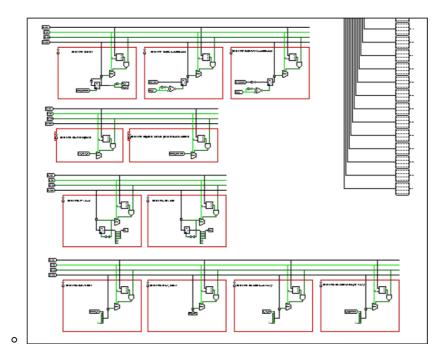


Coordinates bus

Most of circuits work with coordinates Y (row index) and X (bit index) and coordinates go from 2 sources:

- When simulation off they go from keyboard controller which handles user's inputs
- When simulation on they go from 2 I/O registers

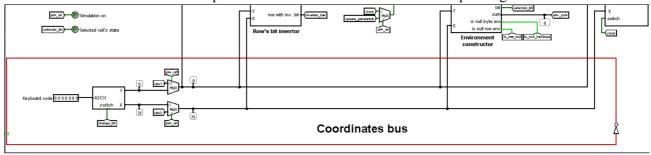
Therefore we use two multiplexers that choose coordinates source depending on simulation state:



Back to table of contents

Controls

Main signals

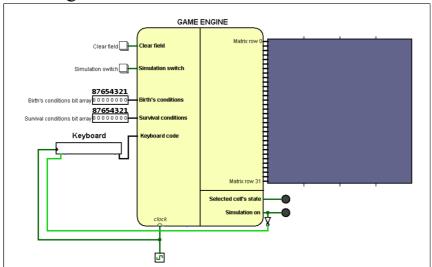

Simulations switch button switches between simulation and setting modes. When we turn from simulation to setting mode we can get unfinished new generation

Two 8-bit inputs let us set different conditions for birth and survival. Bit value 1 on position N means fulfilling of conditions when cell has N neighbors so this inputs represent bit arrays.

Clear button clears all field when simulation is off.

Keyboard Logisim circuit sends keys' ASCII codes to engine. See more below.

On bottom-right side we can see two LED indicators:

- 1. State of cell under the blinking cursor
- 2. Simulation state (when simulation is on indicator will light)

Keyboard

Logisim circuits keyboard handles keys' presses and send 7-bit ASCII codes to Keyboard controller inside engine circuit

All keys are working only while we are in the setting game mode

Keyboard layouts

Cursor moving:

KEY	DIRECTION	X DELTA	Y DELTA
NUM 1/Z	bottom-left	+1	+1
NUM 2/S	bottom	0	+1

KEY	DIRECTION	X DELTA	Y DELTA
NUM 3/C	bottom-right	-1	+1
NUM 4/A	left	+1	0
NUM 6/D	right	-1	0
NUM 7/Q	top-left	+1	-1
NUM 8/W	top	0	-1
NUM 9/E	top-right	-1	-1


Deltas defined as shown above because in matrix top-left cell has X = 31 and Y = 0Cursor position on matrix is marked by blinker

NUM 5 / Space - change state of selected cell in random write buffer using row's bit invertor

Back to table of contents

I/O registers

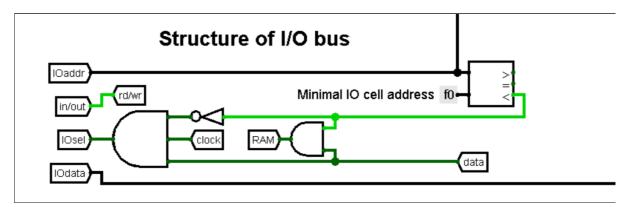I/O bus have minor changes: selection of I/O addresses from CPU addr is detected by less than comparator's output with the second input 0xf0 (the first I/O cell address)



I/O registers' types

All types' names are regarding the CPU directions

Registers have trivial types of data direction: READ ONLY and WRITE ONLY.

PSEUDO WRITE

Besides these types we use one specific type - PSEUDO WRITE. CPU cannot write data to this "registers". Main goal for this type is handle write signal by CdM-8's st instruction.


Short description table

CELL ADDR.	ASSEMBLER LABEL	DATA DIRECTION	EXPLANATION TOPIC	
0xf0	IOGameMode	READ ONLY		
0xf1	IOBirthConditions	READ ONLY	Link	
0xf2	IODeathConditions	READ ONLY	-	
0xf3	IOY	WRITE ONLY	- Link -	
0xf4	IOX	WRITE ONLY		
0xf5	IOBit	READ ONLY		
0xf6	IOEnvSum	READ ONLY	- Link -	
0xf7	IONullRowsEnv	READ ONLY		
0xf8	IONextSignificantX	READ ONLY		
0xf9	IOInvertBitSignal	PSEUDO WRITE	· Link —	
0xfa	IOUpdateGeneration	PSEUDO WRITE	LIIIK	

List with descriptions

Simulation rules

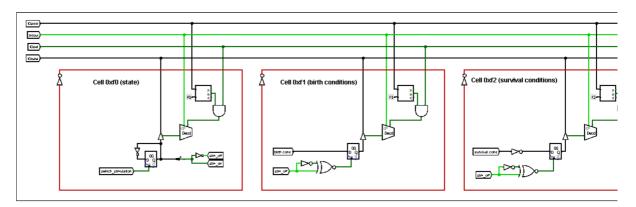
- 0xf0 READ ONLY when simulation off this register will be 0.
 - Trigger signal on this register will invert its value
 - Tunnels from this register are used for control data origins on coordinates bus and some other cases.
- Oxf1 READ ONLY birth conditions as bit array
- Oxf2 READ ONLY death conditions as bit array. This value is inverted version from survival conditions user input



Processed cell

Coordinates from these registers are used in all Logisim components to tell what cell CPU is processing. When simulation on they capture coordinates bus:

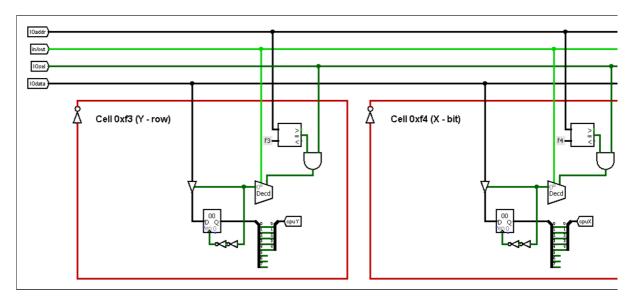
- Oxf3 WRITE ONLY Y coordinate (processing row)
- Oxf4 WRITE ONLY X coordinate (bit index in row)




I/O "registers" with environment data

These "registers" aren't exist. There are just tunnels which are connected to environment constructor outputs:

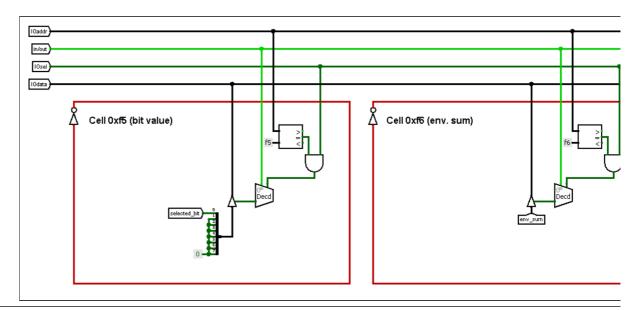
- Oxf5 READ ONLY 1 when bit on position (Y, X) is 1
- Oxf6 READ ONLY sum of bits around cell (Y, X)
- Oxf7 READ ONLY 1 when rows Y-1, Y and Y+1 are null
- 0xf8 READ ONLY next X which satisfy some of conditions:
 - o Cell (Y, X) isn't 0
 - ∘ sum of bits around cell (Y, X) greater than 0



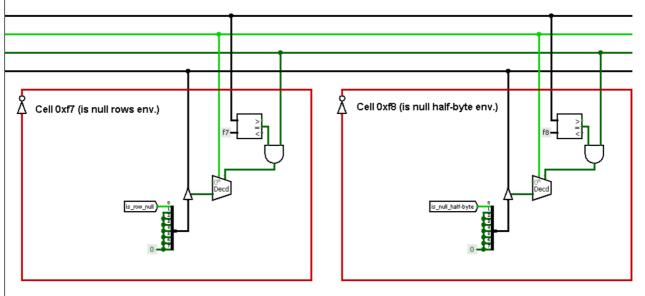

I/O "registers" for changing field

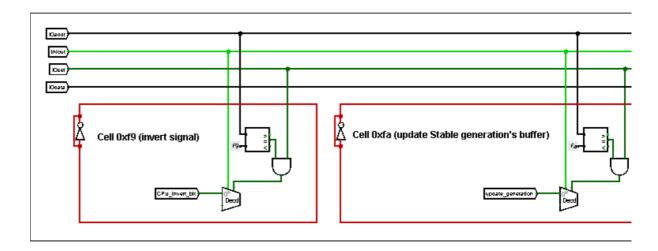- 0xf9 PSEUDO WRITE save signal to this cell will trigger random write buffer and change cell
 (Y, X) using row's bit invertor
- Oxfa PSEUDO WRITE save signal to this cell will update generation buffer



Back to table of contents

Elements description


Keyboard controller

This circuit considers 7-bit ASCII input as ASCII code and compares it with constants related to some keys and make list of actions:

- Cycled increment/decrement X/Y of cursor
- Send switch signal for switching the cell's state


See keyboard layouts here

Circuit screenshot:

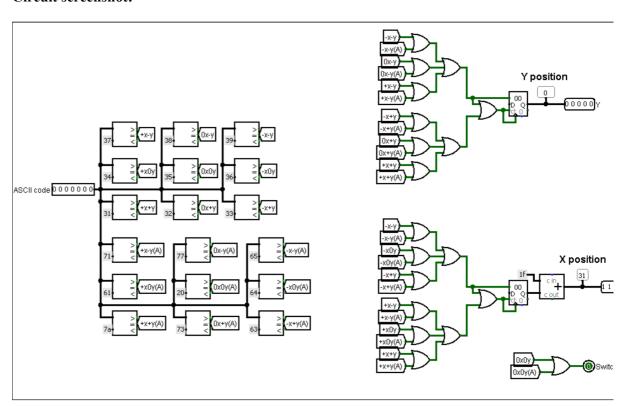

Usage in Engine circuit: Keyboard controller gives user signals that are used while simulation if off:

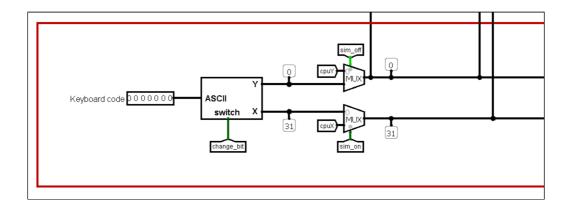- Y and X for [coordinates bus]
- Switch signal which is implemented as Write row in random write buffer



Back to table of contents


Random write buffer


This circuit saves 32-bit row to one of 32 registers and sends all 32 saved rows to outputs.

Trigger for registers is decoder with 5-bit selector Y (row index) and Write row enable input. So, buffer will save row from Input row to Yth register on rising of Write row.

Clear signal resets all registers.

Circuit screenshots:

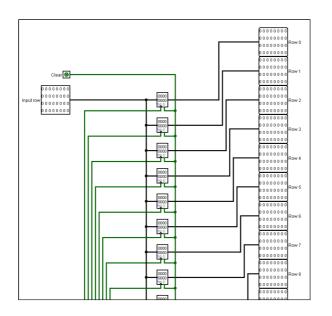

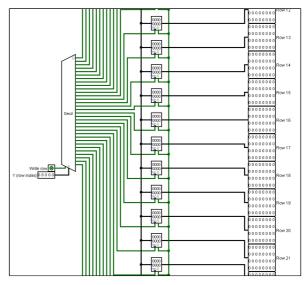


Usage in Engine circuit: In engine we get input row through tunnel from row's bit invertor

Clear signal works while simulation is off.

Y data goes from coordinates bus

Write row signal goes:

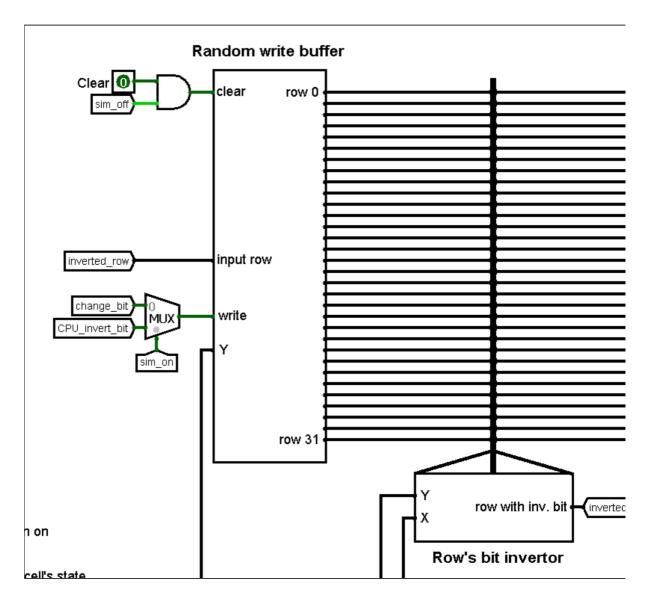- From keyboard controller when simulation is off
- From Register 0xf9 when simulation is on




Back to table of contents

Stable generation's buffer


This buffer just saves 32 32-bit rows from inputs to registers and sends them to 32 outputs. Saving occurs on rising edge of input Save generation trigger

Circuit screenshot:

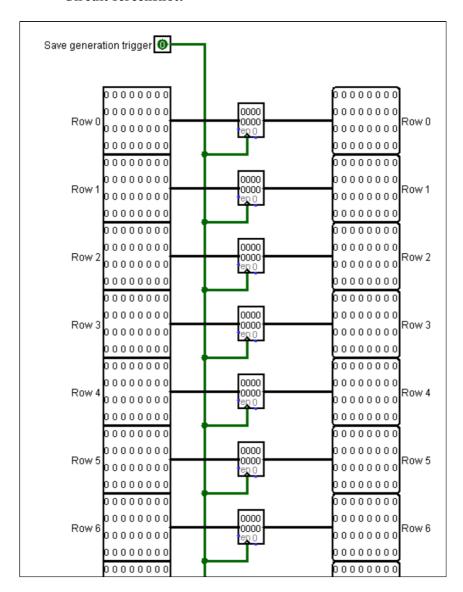

Circuit usage in Engine: Buffer update depends on simulation state:

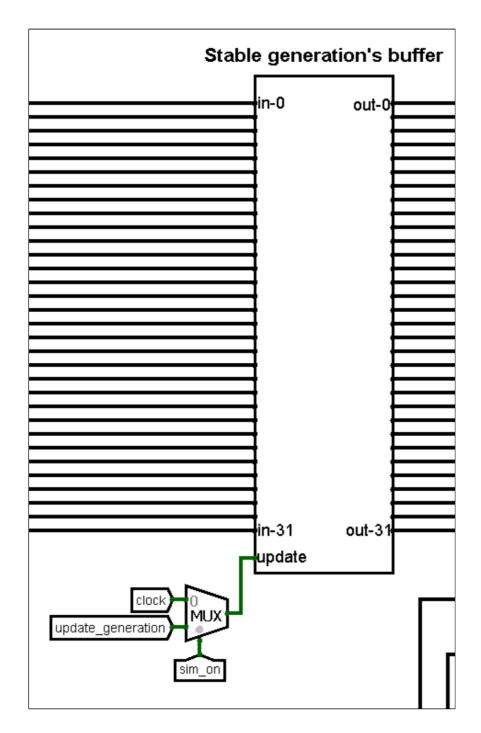- While simulation is off buffer is updated by clock
- While simulation is on buffer is updated after CdM-8 main cycle's full execution by signal from pseudo I/O register




Back to table of contents

Row environment mask

This circuit gets 1 32-bit row and gives 1 32-bit row where i bit is 1 when in input row at least one of i-1, i, i+1 bits is 1 (OR gate on splitter outputs). So, result row let us easily detect bit with significant environment.

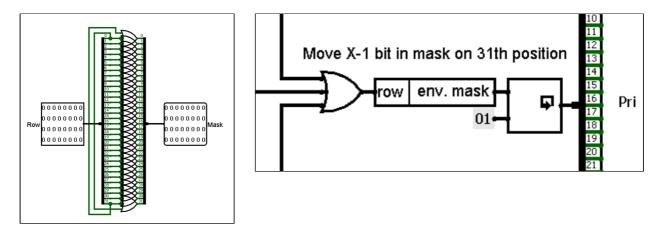Circuit screenshot and usage: this circuit is used in environment data constructor for detecting next X with significant environment by priority encoder.




Environment data constructor

Job of this circuit is constructing data about cell's environment for optimized new generation's counting in CdM-8.

It has 32 32-bit inputs for rows and 5-bit Y, X inputs and works by this steps:

- 1. Get rows Y-1, Y and Y using multiplexers
- 2. Right cycled shift 3 rows on X-1 positions to get X-1, X and X+1 bits on 0, 1 and 2
 - 1. Send bit 1 from middle row to centre bit output
 - 2. Use bits [0,2] from top and bottom rows and bits 0 and 2 from middle row as carry signals for 8 8-bit adders to get sum of cells surrounding centre bit
- 3. Get common row from Y-1, Y and Y+1 rows using OR gate for analyzing environment. It is name environment row
- 4. Construct environment mask from environment row using row environment mask circuit and shift it right on 1 bit to get X-1 bit on 31th position
- 5. This row goes to priority encoder that determines 2 values:
 - 1. If environment mask row is null encoder send true on is row env. null output
 - 2. Index of highest indexed bit which is 1 after sum with X input give us next X with significant environment. This value goes to Next X with significant env.


Circuit screenshots:

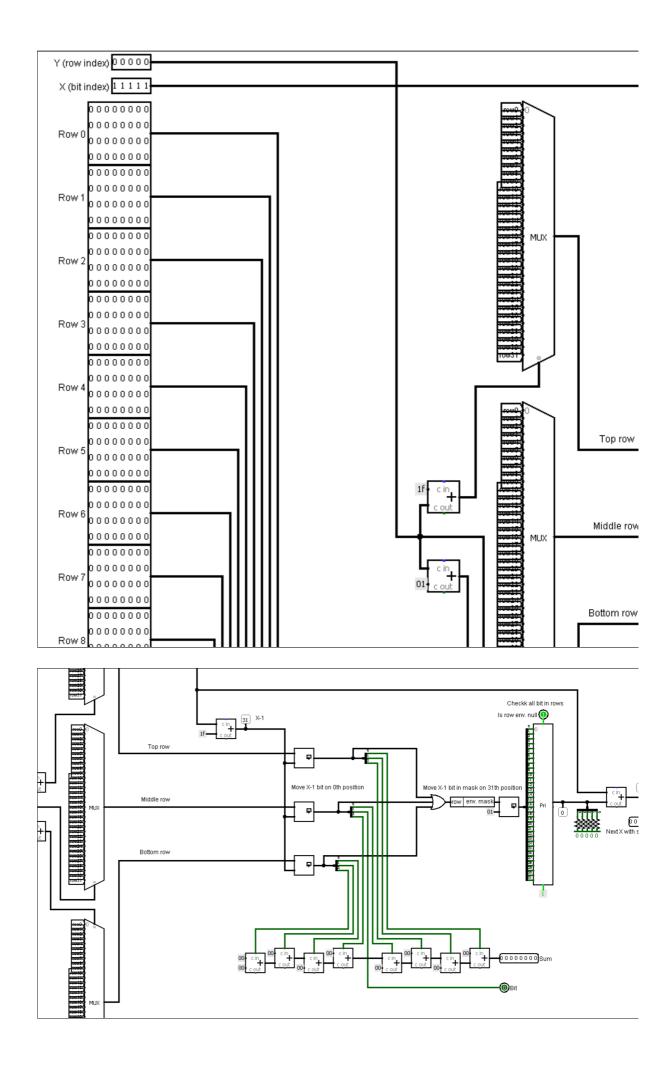

Usage in Engine circuit: Environment data constructor is connected to rows after stable generation's buffer to ensure that CPU works with stable generation.

All outputs go through tunnels to I/O registers that are used in ASM main cycle

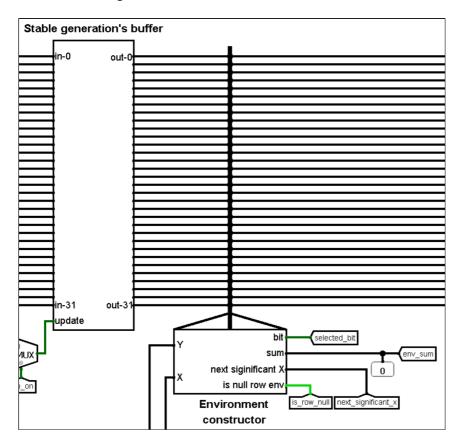Y and X go from coordinates bus but while simulation is off environment data isn't used.




Back to table of contents

Row's bit invertor


This circuit gets 32 32-bit rows and 5 bit coordinates Y and X. Returns Y row with inverted bit on position X. For inversion we use decoder constructed bit mask and XOR

Circuit screenshots:

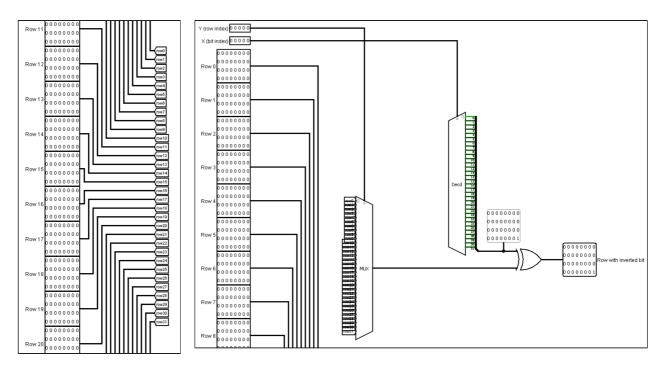

Usage in Engine circuit: 32 input rows goes from random write buffer and inverted row goes through tunnel to input row of random write buffer

Y and X go from coordinates bus

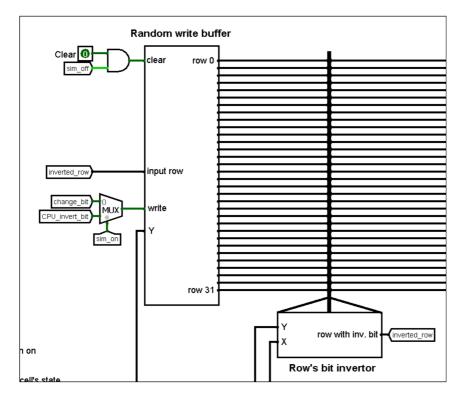

Binary selector

This circuit should choose one of two input values. Binary selector should choose second value if the switch input is 1 and first value otherwise.

Inputs:


• input values: 2 32-bit rows


• switch - 1-bit

Outputs:

• selected value: 1 32-bit row

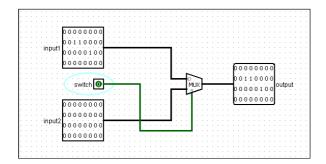Circuit screenshot and its usage: Binary selector is used in blinker for convenient circuit composing.



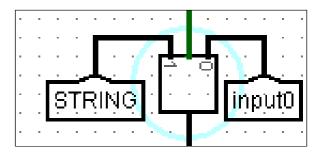

Back to table of contents

Blinker

Blinker must switch value of X bit in Y row to opposite if the switch input is raised and return new row between others unchanged. It is important that this circuit should not store new values in itself.


Inputs:


- matrix rows: 32 32-bit rows
- Y coordinate (row number) 5-bit
- X coordinate (bit number in the row) 5-bit
- switch if this input is raised current bit must switch to opposite

Outputs:


• 32 32-bit outputs, in one of which one bit was changed

Circuit screenshots:

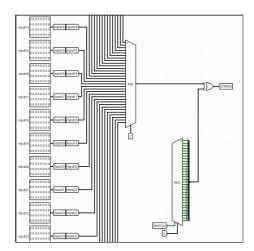

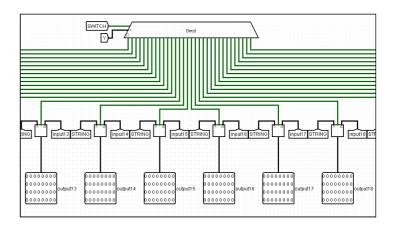

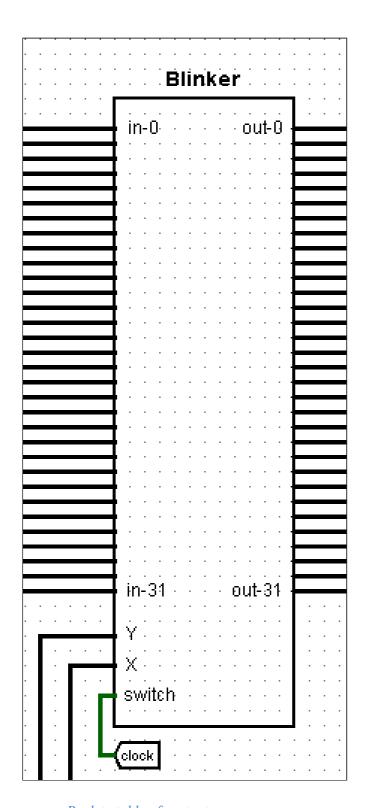Usage in Engine circuit: In switch handles clock signal. Y and X go from coordinates bus



Back to table of contents